


1. 成員

(1) B11130038 王家宏


(2) B11132013 莊東諺

(3) B11132002 蘇志寬

2. Schematic

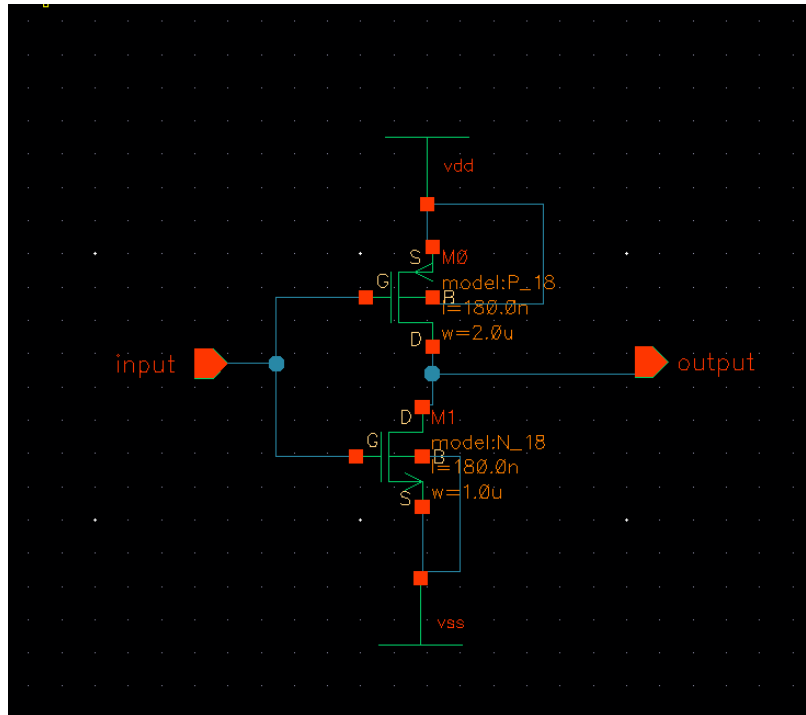

3. Symbolic shape

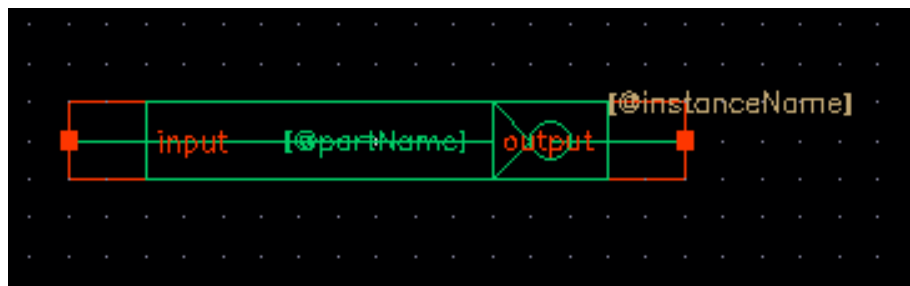

4. SPICE file

```

*****
* auCdl Netlist:
*
* Library Name:  inv
* Top Cell Name: INV
* View Name:     schematic
* Netlisted on:  May 22 22:24:51 2023
*****

*.BIPOLAR
*.RESI = 2000
*.RESVAL
*.CAPVAL
*.DIOPERI
*.DIOAREA
*.EQUATION
*.SCALE METER
*.MEGA
.PARAM
.lib 'hspice.lib' tt
.GLOBAL vdd!
+      vss!

*.PIN vdd!
*+    vss!

*****
* Library Name:  inv
* Cell Name:     INV
* View Name:     schematic
*****

.SUBCKT INV input output
*.PININFO input:I output:0
MM0 output input vdd! vdd! Pch m=1 l=180.0n w=2.0u
MM1 output input vss! vss! Nch m=1 l=180.0n w=1.0u
.ENDS

XINV input output inv

Vvdd vdd! 0 1.8v
Vvss vss! 0 0v
vin input 0 pulse(0v 1.8v 0ns 20ps 20ps 2ns 4ns)

.measure t_rise
+TRIG v(output) VAL=0.18v RISE=1
+TARG v(output) VAL=1.62v RISE=1

.measure t_fall
+TRIG v(output) VAL=1.62v FALL=1
+TARG v(output) VAL=0.18v FALL=1

.measure t_propagation_r
+TRIG v(input) VAL=0.9v FALL=1
+TARG v(output) VAL=0.9v RISE=1

.measure t_propagation_f
"inv.sp" 65L, 1304C written

```

5. slew rate and the propagation delay

```

*****
***** option summary
*****
runlvl = 3          bypass = 2.0000
Opening plot unit= 15
file=inv.pa0

**info** dc convergence successful at Newton-Raphson method
*****
*****
***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is voltage simulation time is 0.
node    =voltage    node    =voltage    node    =voltage

+0:input  = 0.        0:output = 1.8000  0:vdd!   = 1.8000
+0:vss!   = 0.

*****
*****
***** transient analysis tnom= 25.000 temp= 25.000 *****
t_rise= 22.6856p  targ= 2.0595n  trig= 2.0368n
t_fall= 13.0318p  targ= 30.0987p  trig= 17.0669p
t_propagation_r= 13.9747p  targ= 2.0440n  trig= 2.0300n
t_propagation_f= 12.8551p  targ= 22.8551p  trig= 10.0000p

***** job concluded
*****
*****

```

6. waveform

